

浙江大学实验报告

姓名：李彦萱 专业：电子科学与技术 学号：3250100761

课程名称：数字系统 任课老师：李宇波

实验名称：(Prelab)Design On/Off Button (Lab) Design an Electronic Lock 实验日期：2026.3.24

1 实验目的和要求


1.1 实验目的

- (1) Pre lab4:设计和实现 On/off button
- (2) 学习如何利用有限状态机 (FSM) 实现电子锁的控制

1.2 实验要求

Pre lab4:

根据课堂所学的开关按钮功能，实现以下功能

 


- 1) 测试以下代码能否实现

```
module onoff( input button ,output reg light );  
    always @(posedge button) light<= ~light ;  
endmodule
```

- 2) 编写正确的 Verilog 代码，并在板子上实现。（考虑亚稳态问题、抖动问题、脉宽变换）
- 3) 模块中有三个处理子电路。试着去掉其中一部分，测试结果是否正确。

Lab4:

利用学过的知识设计电子锁如下：

 

- 1) 画出 fsm 的状态图。
- 2) 编写 FSM 的行为级 Verilog 模块
- 3) 使用实验 3 中的方法编写一个仿真文件来模拟 FSM。
- 4) 写出上图中整个设计的 Verilog 描述，并在你的 Basys3 板上验证。
- 5) 仅用 D 触发器和 and/OR/NOT 门绘制 FSM 电路。验证你编写的电路和 Vivado 合成的电路。
- 6) 编写 FSM 的 Verilog 模块:对于下一状态逻辑和输出逻辑，用“assign”语句描述组合逻辑，对于 D 触发器，用“always”语句描述。
- 7) 将步骤 2) 中设计的 FSM 模块替换为步骤 2 中设计的 FSM 模块 6)，并在你的电路板上实现整个设计。

2 实验原理

Prelab4:

(1)完整功能需要三级处理电路:

消抖电路:

原理: 通过计数器检测按键电平稳定时间, 过滤掉抖动毛刺, 输出稳定的按键电平信号。

实现: 用系统时钟驱动计数器, 当按键电平持续稳定超过阈值时, 才更新输出状态。

(2)边沿检测电路:

原理: 从稳定后的按键电平中提取上升/下降沿脉冲, 作为一次有效的按键触发信号。

实现: 用两级寄存器打拍, 通过组合逻辑检测电平跳变, 生成一个周期宽的脉冲信号。

(3)状态翻转电路:

原理: 在有效按键脉冲触发下, 翻转 LED 灯的亮灭状态。

实现: 用 D 触发器, 在有效脉冲的上升沿将 light 取反。

Lab4:

电子锁本质是一个有限状态机, 根据输入密码序列和当前状态, 决定下一个状态和输出 (解锁/锁定)

状态编码: 将每个状态映射为二进制编码 (如 S0=000, S1=001...)。

用 D 触发器存储当前状态, 用 AND/OR/NOT 门实现状态转移的组合逻辑, 输出逻辑同样由组合门实现。

与 Vivado 综合后的电路对比, 验证逻辑等价性。


3 实验内容

Pre lab 4:


(1) 测试代码结果: 没有去抖动的代码上板测试, 发现按键输入后, 灯的状态不稳定。(原因: 由于机械触点的弹性作用, 开关在闭合及断开的瞬间均伴随有一连串的抖动, 导致灯的状态不稳定)。

(2) 实现按钮稳定输入的代码编写 (代码赋在实验报告最后)

仿真如图所示:

 


按钮按下后, LED 灯成功亮起, 如图:

 

(3) 去掉其中一部分模块, 发现仿真无法正常稳定运行

lab 4:

(1) 状态机图

 

分析：密码为 01011，状态图如上，在输入上我需要用 3 个按钮分别代表 reset, 0, 1；在输出上我要用一个 LED 亮起代表成功解锁即 unlock=1，用一个数码管的不同状态代表密码输入，即“reset”后数码管显示 0，“0”数码管显示 0，“01”数码管显示 01，以此类推“01011”为显示 5。其中如果下一位输入错误，则根据状态图退回，如在 0101 后输入 0 则退回“3”，而“0”后输入零退回“1”，“01”后输入“1”退回 0，其余类似。

2) 编写 FSM 的行为级 Verilog 模块

代码如下：

```

A. Module top_lock(
    input wire clk,
    input wire reset_btn,
    input wire btn_0,
    input wire btn_1,
    output wire unlock_led,
    output wire [6:0] seg,
    output wire [3:0] an
);
    wire b0_c, b0_p, b1_c, b1_p;

    debounce #(.NDELAY(650000)) d0 (.clk(clk), .reset(reset_btn), .noisy(btn_0), .clean(b0_c));
    pulse p0 (.clk(clk), .in(b0_c), .out(b0_p));

    debounce #(.NDELAY(650000)) d1 (.clk(clk), .reset(reset_btn), .noisy(btn_1), .clean(b1_c));
    pulse p1 (.clk(clk), .in(b1_c), .out(b1_p));

    wire [3:0] step;
    lock_fsm my_fsm
    (.clk(clk), .reset(reset_btn), .btn0_pulse(b0_p), .btn1_pulse(b1_p), .unlock(unlock_led), .state_num(step));
    seg7_decoder my_seg (.num(step), .seg(seg), .seg_en(an));
endmodule

```

```

B. module lock_fsm(
    input clk,

```

```

input reset,
input btn0_pulse,
input btn1_pulse,
output reg unlock,
output reg [3:0] state_num
);
parameter S_RESET = 3'd0, S_1 = 3'd1, S_2 = 3'd2, S_3 = 3'd3, S_4 = 3'd4, S_5 = 3'd5;
reg [2:0] curr, next;

always @(posedge clk or posedge reset) begin
    if (reset) curr <= S_RESET;
    else curr <= next;
end

always @(*) begin
    next = curr;
    if (btn0_pulse) begin
        case(curr)
            S_RESET: next = S_1;
            S_1:     next = S_1;
            S_2:     next = S_3;
            S_3:     next = S_1;
            S_4:     next = S_3;
            S_5:     next = S_1;
        endcase
    end else if (btn1_pulse) begin
        case(curr)
            S_RESET: next = S_RESET;
            S_1:     next = S_2;
            S_2:     next = S_RESET;
            S_3:     next = S_4;
            S_4:     next = S_5;
            S_5:     next = S_RESET;
        endcase
    end
end

always @(*) begin
    unlock = (curr == S_5);
    state_num = {1'b0, curr};
end
endmodule

```

```

C.module debounce #(
    parameter NDELAY =10,
    parameter NBITS = 20
)(
    input wire clk, input wire reset, input wire noisy,
    output reg clean

```

```

);
    reg [NBITS-1:0] count;
    reg xnew;
    always @(posedge clk) begin
        if (reset) begin xnew <= noisy; clean <= noisy; count <= 0; end
        else if (noisy != xnew) begin xnew <= noisy; count <= 0; end
        else if (count == NDELAY) begin clean <= xnew; end
        else begin count <= count + 1; end
    end
Endmodule

```

```

D.module pulse(
    input wire clk,
    input wire in,
    output wire out
);
    reg temp = 0;
    always @(posedge clk) begin
        temp <= in;
    end
    assign out = (~temp) & in;

```

```

Endmodule

```

```

module seg7_decoder(
    input wire [3:0] num,
    output reg [6:0] seg,
    output wire [3:0] seg_en
);

    assign seg_en = 4'b1000;

    always @(*) begin
        case(num)


            4'd0: seg = 7'b0111111;
            4'd1: seg = 7'b0000110;
            4'd2: seg = 7'b1011011;
            4'd3: seg = 7'b1001111;
            4'd4: seg = 7'b1100110;
            4'd5: seg = 7'b1101101;
            default: seg = 7'b0000000;
        endcase
    end
Endmodule

```

3) 仿真实验

A. 密码正确时

仿真输出如图：灯被成功点亮。

 

代码如下：

```
module top_lock_tb();
```

```
    reg clk;
    reg reset_btn; // 对应 S3
    reg btn_0;      // 对应 S2
    reg btn_1;      // 对应 S0
```

```
    wire unlock_led;
    wire [6:0] seg;
    wire [3:0] an;
```

```
    top_lock uut (
        .clk(clk),
        .reset_btn(reset_btn),
        .btn_0(btn_0),
        .btn_1(btn_1),
        .unlock_led(unlock_led),
        .seg(seg),
        .an(an)
    );
```

```
    defparam uut.d0.NDELAY = 10;
    defparam uut.d1.NDELAY = 10;
```

```
    always #5 clk = ~clk;
```

```
    task press_0;
        begin
            btn_0 = 1; #200; // 按下 200ns
            btn_0 = 0; #200; // 松开 200ns
        end
    endtask
```

```
    task press_1;
        begin
            btn_1 = 1; #200;
            btn_1 = 0; #200;
        end
    endtask
```

```

initial begin
    clk = 0;
    reset_btn = 1;
    btn_0 = 0;
    btn_1 = 0;


    #100;
    reset_btn = 0;
    #100;
    press_0(); // 第一位： 0
    press_1(); // 第二位： 1
    press_0(); // 第三位： 0
    press_1(); // 第四位： 1
    press_1(); // 第五位： 1
    #500;

    reset_btn = 1;
    #100;
    reset_btn = 0;

    #1000;
    $stop;
end
endmodule

```

B. 错误密码输入后正确（01101001）
 输出波形图如下：在起初错误输入后

 

代码如下：

```

module top_lock_tb();
    reg clk;
    reg reset_btn;
    reg btn_0;
    reg btn_1;

    wire unlock_led;
    wire [6:0] seg;
    wire [3:0] an;

    top_lock uut (
        .clk(clk),
        .reset_btn(reset_btn),
        .btn_0(btn_0),

```

```

        .btn_1(btn_1),
        .unlock_led(unlock_led),
        .seg(seg),
        .an(an)
    );

```

```

defparam uut.d0.NDELAY = 10;
defparam uut.d1.NDELAY = 10;

```

```

always #5 clk = ~clk;
task press_0;
    begin
        btn_0 = 1; #200;
        btn_0 = 0; #200;
    end
endtask

```

```

task press_1;
    begin
        btn_1 = 1; #200;
        btn_1 = 0; #200;
    end
endtask

```

```

initial begin
    clk = 0; reset_btn = 1; btn_0 = 0; btn_1 = 0;
    #100; reset_btn = 0; #100;
    press_0();
    press_1();
    press_1();


    #600;
    press_0();
    press_1();
    press_0();
    press_1();
    press_1();

    #1000;
    $stop;
end

```

Endmodule

4) 上版实验 (输入 01011)

 

5) 手动计算 FSM，以仅使用 D 触发器和 and/OR/NOT 门绘制 FSM 的电路。


状态			输入 x	次态
S_RESET	000	000	0	001
			1	000
S_1	001	000	0	001
		001	1	010
S_2	010	001	0	011
		010	1	000
S_3	011	010	0	001
		011	1	100
S_4	100	100	0	011
		100	1	101
S_5	101	101	0	001
		101	1	000

$$D_2 = Q_2' Q_1 Q_0 X + Q_2 Q_1' Q_0' X$$

$$D_1 = Q_2' Q_1' Q_0 X + Q_2' Q_1 Q_0' X' + Q_2 Q_1' Q_0' X'$$

$$D_0 = X' + Q_2 Q_1' Q_0' X$$

$$Unlock = Q_2 Q_1' Q_0$$

 

6) 使用时序逻辑和组合逻辑代码实现

```

module lock_fsm(
    input wire clk,
    input wire reset,
    input wire btn0_pulse,
    input wire btn1_pulse,
    output wire unlock,
    output wire [3:0] state_num
);
    reg Q2, Q1, Q0;

    wire D2, D1, D0;
    wire hold = ~(btn0_pulse | btn1_pulse);
    wire N2_0 = 1'b0;
    wire N1_0 = (~Q2 & Q1 & ~Q0) | (Q2 & ~Q1 & ~Q0);
    wire N0_0 = 1'b1;
    wire N2_1 = (~Q2 & Q1 & Q0) | (Q2 & ~Q1 & ~Q0);
    wire N1_1 = (~Q2 & ~Q1 & Q0);
    wire N0_1 = (Q2 & ~Q1 & ~Q0);
    assign D2 = (hold & Q2) | (btn0_pulse & N2_0) | (btn1_pulse & N2_1);
    assign D1 = (hold & Q1) | (btn0_pulse & N1_0) | (btn1_pulse & N1_1);
    assign D0 = (hold & Q0) | (btn0_pulse & N0_0) | (btn1_pulse & N0_1);
    assign unlock = Q2 & ~Q1 & Q0;
    assign state_num = {1'b0, Q2, Q1, Q0};
    always @(posedge clk or posedge reset) begin
        if (reset) begin
            Q2 <= 1'b0;
            Q1 <= 1'b0;
            Q0 <= 1'b0;
        end else begin

```

```


        Q2 <= D2;
        Q1 <= D1;
        Q0 <= D0;
    end
end
Endmodule

module seg7_decoder(
    input  wire [3:0] num,
    output reg  [6:0] seg,
    output wire [3:0] seg_en
);

    assign seg_en = 4'b1000;
    always @(*) begin
        case(num)
            4'd0: seg = 7'b0111111;
            4'd1: seg = 7'b0000110;
            4'd2: seg = 7'b1011011;
            4'd3: seg = 7'b1001111;
            4'd4: seg = 7'b1100110;
            4'd5: seg = 7'b1101101;
            default: seg = 7'b0000000;
        endcase
    end
end
endmodule

```

7) 上板实验

 

4 实验结果和分析

实验顺利完成，结果如上。

5. 心得与体会

本次实验，我更深入地理解了状态机的原理，理解原理、编写程序的能力也得到了提升。起初我在编写程序时经历多次报错，经检查是数码管的引没对齐。后来在第一次成功上板编译时发现所有该不亮的都亮了，该亮的反而都没亮，又经过修改才正常输出。修改代码是一个长期而细致的过程，需要耐性。

附件：原代码

Prelab4:

模块代码:

```
module top_onoff(
    input  wire clk,
    input  wire reset,
    input  wire button_in,
    output reg led_out = 0
);
    // 防止亚稳态
    reg b1, b2;
    always @(posedge clk) begin
        b1 <= button_in;
        b2 <= b1;
    end
    //去抖
    wire b_clean;
    debounce u_debounce (
        .clk(clk),
        .reset(reset),
        .noisy(b2),
        .clean(b_clean)
    );
    //脉宽变换
    wire b_pulse;
    pulse u_pulse (
        .clk(clk),
        .in(b_clean),
        .out(b_pulse)
    );
    //开关翻转逻辑
    always @(posedge clk) begin
        if (reset) led_out <= 0;
        else if (b_pulse) led_out <= ~led_out;
    end
endmodule

module debounce(
    input wire clk,
    input wire reset,
    input wire noisy,
    output reg clean
);
```

```

parameter NDELAY = 10;
parameter NBITS = 20;

reg [NBITS-1:0] count = 0;
reg xnew = 0;

always @(posedge clk) begin
    if (reset) begin
        xnew <= 0; clean <= 0; count <= 0;
    end
    else if (noisy != xnew) begin
        xnew <= noisy;
        count <= 0;
    end
    else if (count == NDELAY) begin
        clean <= xnew; //更新输出
    end
    else begin
        count <= count + 1;
    end
end
Endmodule

```

```

module pulse(
    input wire clk,
    input wire in,
    output wire out
);
    reg temp = 0;
    always @(posedge clk) begin
        temp <= in;
    end
    assign out = in & (~temp);
Endmodule

```

仿真代码：

```

module top_onoff_tb();
    reg clk, reset, button_in;
    wire led_out;
    top_onoff #(NDELAY(10)) uut (
        .clk(clk),
        .reset(reset),
        .button_in(button_in),
        .led_out(led_out)
    );

    always #5 clk = ~clk;

```


initial begin

```
    clk = 0; reset = 1; button_in = 0;
    #20 reset = 0;

    //第一次按下
    #100;
    button_in = 1;
    #10; button_in = 0; #10; button_in = 1; // 模拟抖动
    #400;           // 保持按下状态，观察 led_out 变 1
    button_in = 0;   // 松开按键

    #200;

    // 第二次按下
    button_in = 1;    //按下
    #10; button_in = 0; #10; button_in = 1; //模拟抖动
    #400;           // 保持按下状态，预期观察 led_out 变 0
    button_in = 0;    // 再次松开

    #200;
    $display("Toggle On/Off Test Finished!");
    $stop;
```

end

Endmodule

LAB4

约束文件：

```
# 时钟
set_property PACKAGE_PIN P17 [get_ports clk]
set_property IOSTANDARD LVCNMOS33 [get_ports clk]
# 按钮
set_property PACKAGE_PIN V1 [get_ports reset_btn]
set_property IOSTANDARD LVCNMOS33 [get_ports reset_btn]
set_property PACKAGE_PIN R15 [get_ports btn_0]
set_property IOSTANDARD LVCNMOS33 [get_ports btn_0]
set_property PACKAGE_PIN R11 [get_ports btn_1]
set_property IOSTANDARD LVCNMOS33 [get_ports btn_1]
# 解锁指示灯 LD0
set_property PACKAGE_PIN K3 [get_ports unlock_led]
set_property IOSTANDARD LVCNMOS33 [get_ports unlock_led]
# 数码管段选
set_property PACKAGE_PIN B4 [get_ports {seg[0]}]
set_property IOSTANDARD LVCNMOS33 [get_ports {seg[0]}]
set_property PACKAGE_PIN A4 [get_ports {seg[1]}]
set_property IOSTANDARD LVCNMOS33 [get_ports {seg[1]}]
set_property PACKAGE_PIN A3 [get_ports {seg[2]}]
```

```
set_property IOSTANDARD LVCMOS33 [get_ports {seg[2]}]
set_property PACKAGE_PIN B1 [get_ports {seg[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seg[3]}]
set_property PACKAGE_PIN A1 [get_ports {seg[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seg[4]}]
set_property PACKAGE_PIN B3 [get_ports {seg[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seg[5]}]
set_property PACKAGE_PIN B2 [get_ports {seg[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {seg[6]}]
# 数码管位选
set_property PACKAGE_PIN G2 [get_ports {an[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {an[0]}]
set_property PACKAGE_PIN C2 [get_ports {an[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {an[1]}]
set_property PACKAGE_PIN C1 [get_ports {an[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {an[2]}]
set_property PACKAGE_PIN H1 [get_ports {an[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {an[3]}]
```